

DPP

DAILY PRACTICE PROBLEMS

CLASS : XIITH

DATE :

Solutions

SUBJECT : PHYSICS

DPP NO. : 1

Topic :- Current Electricity

1

(d)

$$\text{Current} = \frac{\text{net emf}}{\text{net resistance}}$$

$$\text{or } I = \frac{2+2+2}{1+1+1+2} = \frac{6}{5} = 1.2A$$

2

(b)

The bridge will be balanced when the shunted resistance of value 2Ω ie, $2 = \frac{3 \times S}{3+S}$. On solving $S = 6\Omega$

4

(a)

Using Wheatstone principle $\frac{P}{Q} = \frac{R}{S} = \frac{R}{100-l}$

$$= \frac{35}{100-35} = \frac{35}{65} = \frac{7}{13}$$

5

(a)

If resistances of bulbs are R_1 and R_2 respectively then in parallel

$$\frac{1}{R_p} = \frac{1}{R_1} + \frac{1}{R_2} \Rightarrow \frac{1}{\left(\frac{V^2}{P_p}\right)} = \frac{1}{\left(\frac{V^2}{P_1}\right)} + \frac{1}{\left(\frac{V^2}{P_2}\right)}$$

$$\Rightarrow P_p = P_1 + P_2$$

6

(c)

Ist case

$$\frac{30}{P+Q} = \frac{l}{(100-l)}$$

$$\frac{30}{30} = \frac{37.5}{37.5}$$

$$\frac{30}{P+Q} = \frac{37.5}{37.5}$$

$$\frac{30}{P+Q} = \frac{62.5}{30 \times 62.5}$$

$$P+Q = \frac{30 \times 62.5}{62.5}$$

$$P+Q = 50 \quad \dots(i)$$

IInd case

$$\frac{30}{PQ} = \frac{l}{(100-l)}$$

$$\frac{30}{P+Q}$$

$$30(P+Q) = \frac{71.4}{(100-71.4)}$$

$$\frac{PQ}{30 \times 50} = \frac{71.4}{(100-71.4)}$$

$$\frac{PQ}{30 \times 50} = \frac{71.4}{28.6}$$

$$PQ = \frac{30 \times 50 \times 28.6}{71.4}$$

$$P \approx 600 \quad \dots(ii)$$



So, from Eqs. (i) and (ii)

$$P = 30\Omega \text{ and } Q = 20\Omega$$

7

(b)

$$r = \left(\frac{l_1 - l_2}{l_2}\right) \times R' = \left(\frac{l_1 - 2}{2}\right) \times 5 \quad \dots(i)$$

$$\text{and } r = \left(\frac{l_1 - 3}{3}\right) \times 10 \quad \dots(ii)$$

on solving (i) and (ii), $r = 10\Omega$

8

(b)

$$\text{No. of ions liberated } (n) = \frac{I \times t}{e \times \text{Valency}(p)}$$

$$ie, n \propto \frac{1}{P}$$

$$\therefore \frac{n_{Ag}}{n_{Al}} = \frac{P_{Al}}{P_{Ag}} = \frac{3}{1}$$

9

(b)

$$\text{Heat produced} = \frac{V^2 t}{R} = mL$$

$$\text{or } m = \frac{V^2}{4.2 R L} = \frac{(210)^2 \times 1}{4.2 \times 50 \times 80} = 2.62 \text{ g}$$

10

(c)

$$S = \frac{i_g G}{(i - i_g)} = \frac{1 \times 0.018}{10 - 1} = \frac{0.018}{9} = 0.002\Omega$$

11

(b)

$$\text{Order of drift velocity} = 10^{-4} \text{ m/sec} = 10^{-2} \text{ cm/sec}$$

12

(c)

Ammeter is always connected in series with circuit

13

(d)

Let (ρ_A, l_A, r_A, A_A) and (ρ_B, l_B, r_B, A_B) are specific resistances, lengths, radii and areas of wires A and B respectively.

Resistance of

$$A = R_A = \frac{\rho_A l_A}{A_A} = \frac{\rho_A l_A}{\pi r_A^2}$$

Resistance of

$$B = R_B = \frac{\rho_B l_B}{A_B} = \frac{\rho_B l_B}{\pi r_B^2}$$

For given information

$$\rho_B = 2\rho_A$$

$$r_B = 2r_A$$

$$\text{And } R_A = R_B$$

$$\therefore \frac{\rho_A l_A}{\pi r_A^2} = \frac{\rho_B l_B}{\pi r_B^2}$$

$$\Rightarrow \frac{\rho_A l_A}{\pi r_A^2} = \frac{2\rho_A \times l_B}{\pi (2r_A)^2}$$

$$\Rightarrow \frac{l_B}{l_A} = \frac{2}{1} = 2:1$$

14

(b)

$$P = \frac{V^2}{R} \Rightarrow \frac{P_1}{P_2} = \frac{R_2}{R_1} \Rightarrow \frac{6}{P_2} = \frac{4}{6} = \frac{2}{3} \Rightarrow P_2 = 9 \text{ W}$$

15

(a)

An ideal cell has zero resistance

16

(c)

$$i = q/t = ne/t$$



or $n = it/e = \frac{2 \times 1}{1.6 \times 10^{-19}} = 1.25 \times 10^{19}$

17

(b)

In parallel $P_{consumed} \propto \text{Brightness} \propto \frac{1}{R}$

$P_A > P_B$ [Given] $\therefore R_A < R_B$

18

(d)

$$I = \frac{P}{V} = \frac{10^5}{200} = 500 \text{ A}$$


and $W = zlt = 0.367 \times 10^{-3} \times 500 \times 1 = 0.1835 \text{ g}$

19

(a)

Equivalent resistance of the combination
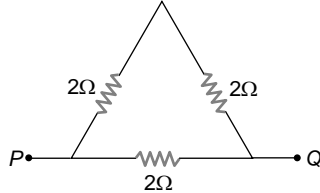
$$= \frac{(2 + 2) \times 2}{2 + 2 + 2} = \frac{8}{6} = \frac{4}{3} \Omega$$



20

(d)

Resistance of a conductor varies linearly with temperature as

$$R_t = R_0(1 + \alpha t)$$

For the first conductor

$$R_{t_1} = R_0(1 + \alpha_1 t_1)$$

$$\text{or } \alpha_1 = \frac{R_{t_1} - R_0}{t} \dots (i)$$

Similarly, for second conductor

$$\alpha_2 = \frac{R_{t_2} - R_0}{t_2} \dots \dots (ii)$$

From Eq. (i) and Eq. (ii), we get

$$\frac{\alpha_1}{\alpha_2} = \frac{t_2}{t_1}$$

| ANSWER-KEY | | | | | | | | | | |
|------------|----|----|----|----|----|----|----|----|----|----|
| Q. | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 | 9 | 10 |
| A. | D | B | A | A | A | C | B | B | B | C |
| | | | | | | | | | | |
| Q. | 11 | 12 | 13 | 14 | 15 | 16 | 17 | 18 | 19 | 20 |
| A. | B | C | D | B | A | C | B | D | A | D |
| | | | | | | | | | | |



**SMARTLEARN
COACHING**