

## DPP

DAILY PRACTICE PROBLEMS

Class : XII<sup>th</sup>  
Date :

Solutio

Subject : PHYSICS  
DPP No. : 1

### Topic :- Alternating current

1

(b)

$$e = 300\sqrt{2} \sin \omega t$$

$$I_0 = \frac{e_0}{Z} = \frac{300\sqrt{2}}{\sqrt{(30)^2 + (10 - 10)^2}}$$

{ $\because Z = \sqrt{R^2 + (X_L - X_C)^2}$ }

$$= \frac{300\sqrt{2}}{30} = 10\sqrt{2} \text{ A}$$

$\therefore$  Current  $I = \frac{I_0}{\sqrt{2}} = 10 \text{ A}$

2

(a)

Natural frequency is nothing but resonant frequency.

In this case  $X_L = X_C$

$$\Rightarrow \omega_0 L = \frac{1}{\omega_0 C}$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow 2\pi f = \frac{1}{\sqrt{LC}}$$

$$\Rightarrow f = \frac{1}{2\pi\sqrt{LC}}$$

3

(a)

At angular frequency  $\omega$ , the current in  $RC$  circuit is given by

$$i_{rms} = \frac{V_{rms}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} \dots (i)$$

$$\text{Also } \frac{i_{rms}}{2} = \frac{V_{rms}}{\sqrt{R^2 + \left(\frac{1}{\omega C}\right)^2}} = \frac{V_{rms}}{\sqrt{R^2 + \frac{9}{\omega^2 C^2}}} \dots (ii)$$

From equation (i) and (ii), we get

$$3R^2 = \frac{5}{\omega^2 C^2} \Rightarrow \frac{1}{\omega C} = \sqrt{\frac{3}{5}} \Rightarrow \frac{X_C}{R} = \sqrt{\frac{3}{5}}$$

4

(d)

$$\text{Resistance of coil}(R) = \frac{200}{1} = 200 \Omega$$

$$\text{Current, } I = \frac{200}{\sqrt{R^2 + X_L^2}}$$

$$\text{or } 0.5 = \frac{200}{\sqrt{R^2 + X_L^2}}$$

$$\text{or } R^2 + (2\pi fL)^2 = (400)^2$$

$$\text{or } \left(2\pi f \times \frac{2\sqrt{3}}{\pi}\right)^2 = (400)^2 - (200)^2$$

$$= 120000$$

$$\text{or } 4f\sqrt{3} = 200\sqrt{3}$$

$$\text{or } f = 50 \text{ Hz}$$

5 (a)

$\cos \phi = \frac{R}{Z}$ . In choke coil  $\phi = 90^\circ$  so  $\cos \phi \approx 0$

6 (b)

$$Q\text{-factor} = \frac{1}{R} \sqrt{\frac{L}{C}} = \frac{1}{6} \sqrt{\frac{1}{17.36 \times 10^{-6}}} = 40$$

7 (a)

$$P = E_{rms} i_{rms} \cos \phi = \frac{E^2 R}{Z^2} = \frac{E^2 R}{\left[R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2\right]}$$

8 (b)

$$R = \frac{P}{i_{rms}^2} = \frac{240}{16} = 15\Omega; Z = \frac{V}{i} = \frac{100}{4} = 25\Omega$$

$$\text{Now } X_L = \sqrt{Z^2 - R^2} = \sqrt{(25)^2 - (15)^2} = 20\Omega$$

$$\therefore 2\pi\nu L = 20 \Rightarrow L = \frac{20}{2\pi \times 50} = \frac{1}{5\pi} \text{ Hz}$$

9 (b)

$$P = \frac{1}{2} V_0 i_0 \cos \phi \Rightarrow P = P_{peak} \cdot \cos \phi$$

$$\Rightarrow \frac{1}{2} (P_{peak}) = P_{peak} \cos \phi \Rightarrow \cos \phi \frac{1}{2} \Rightarrow \phi = \frac{\pi}{3}$$

10 (d)

When a ring moves in a magnetic field in a direction perpendicular to its plane, we replace the ring by a diameter ( $2r$ ) perpendicular to the direction of motion. The emf is induced across this diameter. Current flow in the ring will be through the two semicircular portions in parallel.

Induced emf =  $B(2r)v$ .

Resistance of each half of ring =  $R/2$

As the two halves are in parallel, therefore, equivalent resistance =  $R/4$

$$\therefore \text{Current in the section} = \frac{B(2r)v}{R/4}$$

$$I = \frac{8Brv}{R}$$

13 (c)

$$Z = \sqrt{R^2 + \left(2\pi fL - \frac{1}{2\pi fC}\right)^2}$$

From above equation at  $f = 0, z = \infty$

When  $f = \frac{1}{2\pi\sqrt{LC}}$  (resonant frequency)  $\Rightarrow Z = R$

For  $f > \frac{1}{2\pi\sqrt{LC}} \Rightarrow Z$  starts increasing

*i. e.*, for frequency  $0 - f_r, Z$  decreases and for  $f_r$  to  $\infty, Z$  increases

This is justified by graph c

14

(a)

$$X_C = \frac{1}{2\pi\nu C} \Rightarrow \frac{1}{1000} = \frac{1}{2\pi \times \nu \times 5 \times 10^{-6}}$$

$$\Rightarrow \nu = \frac{100}{\pi} \text{ MHz}$$

15

(a)

$$i_{rms} = \frac{i_0}{\sqrt{2}} = \frac{5}{\sqrt{2}} = 3.536 \text{ A}$$

16

(a)

$$X_L = \omega L.$$

$$\text{or } L = \frac{X_L}{\omega} = \frac{10}{20} = 0.5 \text{ H}$$

17

(b)

When a circuit contains inductance only, then the current lags behind the voltage by the phase difference of  $\frac{\pi}{2}$  or  $90^\circ$ .

While in a purely capacitive circuit, the current leads the voltage by a phase angle of  $\frac{\pi}{2}$  or  $90^\circ$ .

In a purely resistive circuit current is in phase with the applied voltage.

18

(b)

At  $t = 0$ , inductor behaves like an infinite resistance. So at

$$t = 0, i = \frac{V}{R_2}$$

And at  $t = \infty$ , inductor behaves like a conducting wire,

$$i = \frac{V}{R_{eq}} = \frac{V(R_1 + R_2)}{R_1 R_2}$$


19

(c)


Hot wire ammeter reads *rms* value of current. Hence its peak value =  $i_{rms} \times \sqrt{2} = 14.14 \text{ amp}$

20

(c)

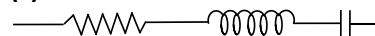


$$\frac{X_C}{R} = \tan \frac{\pi}{3}$$

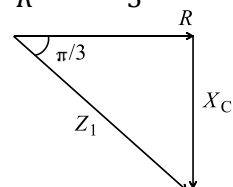

$$X_C = R \tan \frac{\pi}{3} \quad \dots (i)$$

$$\frac{X_L}{R} = \tan \frac{\pi}{3}$$

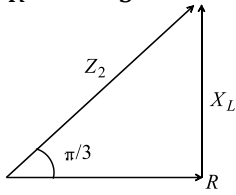

$$X_L = R \tan \frac{\pi}{3} \quad \dots \text{(ii)}$$

$$\text{Net impedance } Z = \sqrt{R^2 + (X_L - X_C)^2} = R$$

$$\text{Power factor } \cos \phi = \frac{R}{Z} = 1$$

### ANSWER-KEY

Q.	1	2	3	4	5	6	7	8	9	10
A.	B	A	A	D	A	B	A	B	B	D
Q.	11	12	13	14	15	16	17	18	19	20
A.	C	D	C	A	A	A	B	B	C	C

**SMARTLEARN  
COACHING**