

## DPP

DAILY PRACTICE PROBLEMS

CLASS : XII<sup>TH</sup>

DATE :

### Solutions

SUBJECT : PHYSICS

DPP NO. : 2

### Topic :- Current Electricity

1

(a)

Ammeter is always connected in series and voltmeter in parallel.

2

(a)

$$S = \frac{G}{\frac{1}{i_g} - 1} = \frac{25}{\frac{5}{50 \times 10^{-6}} - 1} = \frac{25}{10^5 - 1} = \frac{25}{10^5} = 2.5 \times 10^{-4} \Omega$$

3


(a)

$$\begin{aligned} \text{Potential gradient} &= \frac{V}{L} = \frac{iR}{L} = \frac{i\rho L}{AL} = \frac{i\rho}{A} \\ &= \frac{0.2 \times 40 \times 10^{-8}}{8 \times 10^{-6}} = 10^{-2} \text{V/m} \end{aligned}$$

4

(c)

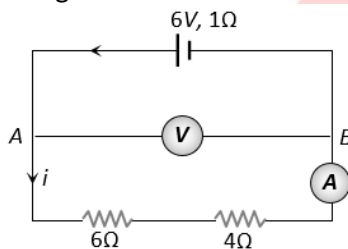The given circuit can be redrawn as follows



$$\text{Current } i = \frac{6}{6+4+1} = \frac{6}{11} \text{A}$$

$$\text{P.D. between A and B, } V = \frac{6}{11} \times 10 = \frac{60}{11} \text{V}$$

5

(b)

$$1 \text{ division} = 1 \mu\text{A}$$

$$\text{Current for } 1^\circ\text{C} = \frac{40 \mu\text{V}}{10} = 4 \mu\text{A}$$

$$1 \mu\text{A} = \frac{1}{4} ^\circ\text{C} = 0.25^\circ\text{C}$$

6

(a)

Two resistances of each side of triangle are connected in parallel. Therefore, the effective resistance of each arm of the triangle would be  $= \frac{r \times r}{r+r} = \frac{r}{2}$ . The two arms AB and AC are in series and they together are in parallel with third one.

$$\therefore R'(r/2) + (r/2) = r$$

Total resistance

$$\frac{1}{R} = \frac{1}{r} + \frac{2}{r} = \frac{3}{r}$$

$$R = r/3$$

7

(d)

$$I = neAv_d$$



$$\text{or } v_d = \frac{1}{neA}$$

$$\text{or } v_d \propto \frac{I}{A}$$

$$\therefore \frac{v'd}{vd} = \frac{I'/A'}{I/A} = \frac{2I/2A}{I/A} = 1$$

$$\text{or } v'd = v_d = v$$

8 (d)

Let the resistance of the wire be  $R$ , then we know that resistance is proportional to the length of the wire. So each of the four wires will have  $R/4$  resistance and they are connected in parallel. So the effective resistance will be

$$\frac{1}{R_1} = \left(\frac{4}{R}\right) \Rightarrow R_1 = \frac{R}{16}$$

9 (b)

By Faraday's law,  $m \propto it$

$$\therefore \frac{m_1}{m_2} = \frac{i_1 t_1}{i_2 t_2} \Rightarrow \frac{m}{m_2} = \frac{4 \times 120}{6 \times 40} \Rightarrow m_2 = \frac{m}{2}$$

10 (d)

1 coulomb  $\times$  1 volt = 1 joule

Hence, option (d) is incorrect.

11 (a)

$$\frac{i}{i_g} = 1 + \frac{G}{S} \Rightarrow \frac{i}{V_g} = 1 + \frac{G}{S} \Rightarrow \frac{100 \times 10^{-3} \times 40}{800 \times 10^{-3}} = 1 + \frac{40}{S}$$

$$\Rightarrow S = 10\Omega$$

12 (a)

This is a balanced Wheatstone bridge. Therefore no current will flow from the diagonal resistance  $10\Omega$

$$\therefore \text{Equivalent resistance} = \frac{(10+10) \times (10+10)}{(10+10) + (10+10)} = 10\Omega$$

13 (a)

$$E = at + \frac{1}{2}bt^2 \quad \dots (i)$$

Differentiating Eq. (i), w.r.t.,  $t$

We have

$$\frac{dE}{dt} = a + bt$$

When  $t = t_n$ , i.e., neutral temperature, then

$$\frac{dE}{dt} = 0$$

$$\therefore 0 = a + bt_n \text{ or } t_n = -\frac{a}{b}$$

The temperature of inversion

$$t_i = 2t_n = t_0$$

$$= 2t_n - 0 = -\frac{2a}{b}$$

Thermoelectric power

$$P = \frac{dE}{dt} = a + bt$$

14 (c)

Since, charge ( $q$ ) = current ( $i$ )  $\times$  times ( $t$ )

Therefore, charge is equal to area under the curve.

$$\therefore \text{Ist rectangle} = q = lb = 2$$

$$\text{IInd rectangle} = q = lb = 2$$

IIIrd triangle =  $q = \frac{1}{2}lb = 2$

Hence, ratio is 1:1:1.

15

**(b)**

The internal resistance of battery is given by

$$r = \left(\frac{E}{V} - 1\right)R = \left(\frac{40}{30} - 1\right) \times 9 = \frac{9 \times 10}{30} = 3\Omega$$

16

**(a)**

Conductivity  $\sigma = \frac{1}{\rho}$  ... (i)

and conductance  $G = \frac{1}{R}$

$\Rightarrow GR = 1$  ... (ii)

From equation (i) and (ii)  $\sigma = \frac{GR}{\rho}$

18

**(d)**

Let the current in  $12\Omega$  resistance is  $i$

Applying loop theorem in closed mesh  $AEFCA$

$12i = -E + E = 0$

$\therefore i = 0$

19

**(b)**

$$P \propto V^2 \Rightarrow \frac{P}{P_0} = \left(\frac{V}{V_0}\right)^2 \Rightarrow P = \left(\frac{V}{V_0}\right)^2 P_0$$

20

**(a)**

$$P = \frac{V^2}{R} \Rightarrow \frac{P_P}{P_S} = \frac{R_S}{R_P} = \frac{(R_1 + R_2)}{R_1 R_2 / (R_1 + R_2)} = \frac{(R_1 + R_2)^2}{R_1 R_2}$$

$$\Rightarrow \frac{100}{25} = \frac{(R_1 + R_2)^2}{R_1 R_2} \Rightarrow \frac{R_1}{R_2} = \frac{1}{1}$$

ANSWER-KEY										
Q.	1	2	3	4	5	6	7	8	9	10
A.	A	A	A	C	B	A	D	D	B	D
Q.	11	12	13	14	15	16	17	18	19	20
A.	A	A	A	C	B	A	A	D	B	A



**SMARTLEARN  
COACHING**