

DPP

DAILY PRACTICE PROBLEMS

CLASS : XIITH
DATE :


Solutions

SUBJECT : PHYSICS
DPP NO. : 3

Topic :- Current Electricity

1 (c)
For semiconductors, resistance decreases on increasing the temperature

2 (b)
Given circuit is equivalent to

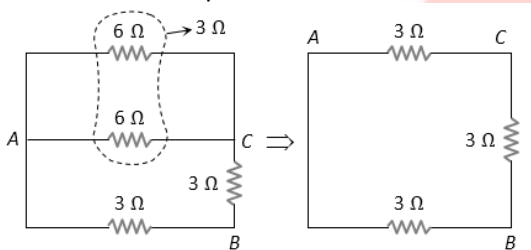

So the equivalent resistance between points A and B is equal to

$$R = \frac{6 \times 3}{6 + 3} = 2\Omega$$

3 (d)
Energy consumed in kWh = $\frac{\text{watt} \times \text{hour}}{1000}$
 \Rightarrow For 30 days, $P = \frac{10 \times 50 \times 10}{1000} \times 30 = 150 \text{ kWh}$

4 (a)
Ammeter is always connected in series and Voltmeter is always connected in parallel

5 (c)

$$It = \frac{m}{z} = \frac{5 \times 10^{-3}}{3.387 \times 10^{-7}}$$

$$= \frac{5 \times 10^4}{3.387 \times 60 \times 60} \text{ Ah} = 4.1 \text{ Ah}$$


6 (d)

$$\frac{R_1}{R_2} = \frac{(1 + \alpha t_1)}{(1 + \alpha t_2)} \Rightarrow \frac{5}{6} = \frac{(1 + \alpha \times 50)}{(1 + \alpha \times 100)} \Rightarrow \alpha = \frac{1}{200} \text{ per } ^\circ\text{C}$$
 Again by $R_t = R_0(1 + \alpha t)$

$$\Rightarrow 5 = R_0 \left(1 + \frac{1}{200} \times 50 \right) \Rightarrow R_0 = 4\Omega$$


7 (d)

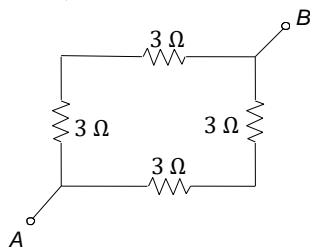Given, the resistance of wire $R=12\Omega$. The wire is bent in square form



$$R_1 = 3 + 3 = 6\Omega$$

$$R_2 = 3 + 3 = 6\Omega$$

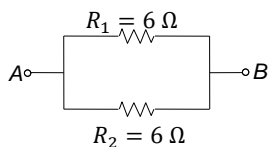

$$\frac{1}{R'} = \frac{1}{6} + \frac{1}{6}$$

$$\text{or } \frac{1}{R'} = \frac{2}{6}$$

$$\text{or } R' = 3\Omega$$

8

(a)

$$\text{Chemical equivalent of gold} = \frac{197.1}{3} = 65.7$$

$$\text{Gold to be deposited} = \frac{200 \times 5}{100} = 10\text{g}$$

Electrochemical equivalent of gold

$$z_2 = \frac{W_2}{W_1} z_1 \quad z_2 = \frac{65.7}{1.008} \times 0.1044 \times 10^{-4} \text{gC}^{-1}$$

$$\text{Also } m = zlt, t = \frac{m}{zl}$$

$$\Rightarrow = \frac{10}{\left(\frac{65.7}{1.008} \times 0.1044 \times 10^{-4} \times 2\right)}$$

$$= 7347.9\text{s}$$

9

(d)


$$I^2 \times 6 = 60 \text{ or } I = \sqrt{10} \text{ A}$$

Current through upper branch = $2\sqrt{10}$ A. Heat produced per second $3\Omega =$

$$(2\sqrt{10})^2 \times 3 \text{ cal} = 120 \text{ cal.}$$

10

(c)

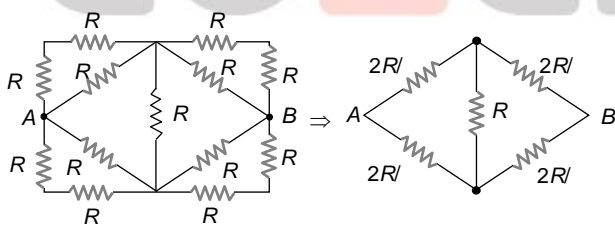

Hence $R_{eq} = \frac{2R}{3}$ [Since it's a balanced Wheatstone bridge]

11

(d)

Because cell is in open circuit



14

(c)

$$v_d = \frac{I}{nAe} = \frac{20}{10^{29} \times 10^{-6} \times 1.6 \times 10^{-19}} = 1.25 \times 10^{-3} \text{ m/s}$$

15

(b)

Let R be the resistance of each lamp and V be the voltage supplied to the circuit. Current in the circuit is

$$I_1 = \frac{V}{R + \frac{R \times R}{R+R}} = \frac{2V}{3R}$$

Current flowing through B or C ,

$$I_2 = \frac{I_1}{2} = \frac{1}{2} \left(\frac{2V}{3R} \right) = \frac{V}{3R}$$

When C is fused, the whole current flows through A and B .

Then, $I'_2 = V/2R$

So current through A decreases and current through B increases. Therefore brilliance of A decreases and that of B increase.

16

(c)

As for an electric appliance $R = \frac{V^2}{P}$.

For first bulb, its resistance

$$R_1 = \frac{V^2}{P_1} = \frac{250 \times 250}{100} = 625 \Omega$$

For second bulb, its resistance

$$R_2 = \frac{V_2^2}{P_2} = \frac{200 \times 200}{100} = 400 \Omega$$

Now, in series potential divides in proportion to resistance.

$$\text{So, } V_2 = \frac{R_2}{(R_1 + R_2)} V$$

Where V is supply voltage.

\therefore Potential drop across bulb B_2 .

$$\begin{aligned} V_2 &= \frac{400}{(625 + 400)} \times 250 \\ &= 97.56 \text{ V} \\ &= 98 \text{ V} \end{aligned}$$

17

(d)

Equivalent weight of aluminium = $\frac{27}{3} = 9$


So 1 faraday = 96500 C are required to liberate 9 gm of Al

18

(a)

In the following circuit potential difference between

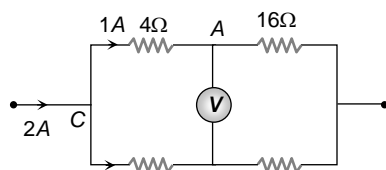C and A is $V_C - V_A = 1 \times 4 = 4 \dots(i)$



C and B is $V_C - V_B = 1 \times 16 = 16 \dots(ii)$

On solving equations (i) and (ii) we get


$$V_A - V_B = 12V$$



19

(a)

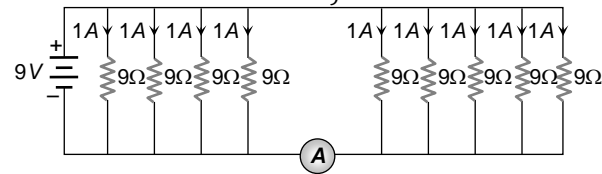Equivalent resistance $R = \frac{9}{9} = 1\Omega$



Current $i = \frac{9}{1} = 9A$

Current passing through the ammeter = 5A

20

(b)

$$\text{Power, } P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P} = \frac{(60)^2}{160} = 22.5\Omega$$

Now, according to Ohm's law

$$V = IR$$

$$\therefore I = \frac{60}{22.5}$$


$$\Rightarrow I = 2.6A$$

Here, $t = 60s$

$$\text{As } I = \frac{ne}{t}$$

$$\Rightarrow n = \frac{I \times t}{e}$$
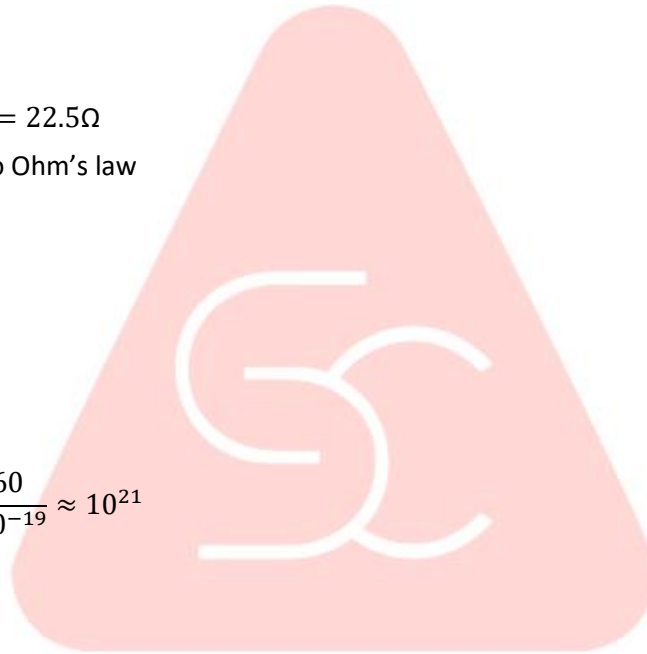
$$= \frac{2.6 \times 60}{1.6 \times 10^{-19}} \approx 10^{21}$$



SMARTLEARN
COACHING

ANSWER-KEY



Q.	1	2	3	4	5	6	7	8	9	10
A.	C	B	D	A	C	D	D	A	D	C
Q.	11	12	13	14	15	16	17	18	19	20
A.	D	C	B	C	B	C	D	A	A	B



SMARTLEARN
COACHING