

DPP

DAILY PRACTICE PROBLEMS

Class : XIIth

Date :

Solutio

Subject : PHYSICS

DPP No. : 3

Topic :- Alternating current

1

(b)

$$Z = \sqrt{R^2 + X_L^2}, X_L = \omega L \text{ and } \omega = 2\pi f$$

$$\therefore Z = \sqrt{R^2 + 4\pi^2 f^2 L^2}$$

3


(b)

$$V_{rms} = \frac{V_0}{\sqrt{2}} = \frac{120}{1.414} = 84.8 \text{ V}$$

4

(a)

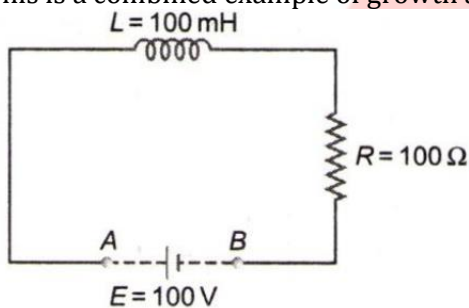This is a combined example of growth and decay of current in an $L - R$ circuit.




The current through circuit just before shorting the battery,

$$I_0 = \frac{E}{R} = 1 \text{ A}$$

(as inductor would be shorted in steady state)

After this decay of current starts in the circuit according to the equation $I = I_0 e^{-t/\tau}$

Where $\tau = L/R$.

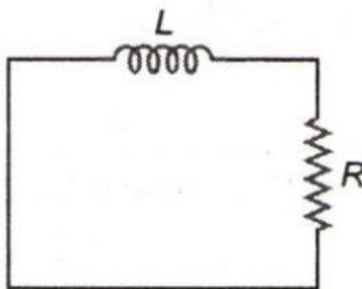

$$I = 1 \times e^{-(1 \times 10^{-3}) / (100 \times 10^{-3} / 100)} = (1/e) \text{ A}$$

5

(d)

$$\frac{R}{L} = \frac{e/i}{ed t/di} = \frac{1}{at} = \text{frequency.}$$

6

(a)

Phase difference relative to the current

$$\phi = \left(314t - \frac{\pi}{6}\right) - (314t) = -\frac{\pi}{6}$$

7

(b)



At $t = 0$, phase of the voltage is zero, while phase of the current is $-\frac{\pi}{2}$, i. e., voltage leads by $\frac{\pi}{2}$

8

(d)

$$\begin{aligned} Z^2 &= R^2 + (2\pi fL)^2 \\ &= (30)^2 + \left(2\pi \times 50 \times \frac{0.4}{\pi}\right)^2 \\ &= (900 + 1600) = 2500 \end{aligned}$$

or $Z = 50 \Omega$

Also, $I = \frac{V}{Z} = \frac{200}{50} = 4 \text{ A}$

10

(b)

We know that Q - factor of series resonant circuit is given as

$$Q = \frac{\omega_r L}{R}$$

Here, $L = 8.1 \text{ mH}$, $C = 12.5 \mu\text{F}$, $R = 10 \Omega$, $f = 500 \text{ Hz}$

$$\begin{aligned} \therefore Q &= \frac{\omega_r L}{R} = \frac{2\pi fL}{R} \\ &= \frac{2 \times \pi \times 500 \times 8.1 \times 10^{-3}}{10} = \frac{8.1\pi}{10} = 2.5434 \end{aligned}$$

11

(b)

For capacitive circuits $X_C = \frac{1}{\omega C}$

$$\therefore i = \frac{V}{X_C} = V\omega C \Rightarrow i \propto \omega$$

12

(b)

$$V_0 = \sqrt{2} V_{rms} = 10\sqrt{2}$$

13

(a)

In L-R circuit, the growing current at time t is given by $i = i_0 \left[1 - e^{-\frac{t}{\tau}}\right]$ where $i_0 = \frac{E}{R}$ and $\tau = \frac{L}{R}$

\therefore Charge passed through the battery in one time constant is

$$\begin{aligned} q &= \int_0^{\tau} i dt = \int_0^{\tau} i_0 (1 - e^{-t/r}) dt \\ q &= i_0 \tau - \left[\frac{i_0 e^{-t}}{-2/\tau} \right]_0^{\tau} = i_0 \tau + i_0 \tau [e^{-1} - 1] \\ &= i_0 \tau - i_0 \tau + \frac{i_0 \tau}{e} \\ q &= \frac{i_0 \tau}{e} = \frac{(E/R)(L/R)}{e} = \frac{eL}{eR^2} \end{aligned}$$

14

(b)

$$P_i = 240 \times 0.7 = 168 \text{ W}, P_0 = 140 \text{ W}$$

$$\eta = \frac{P_0}{P_i} \times 100 = \frac{140}{168} \times 100 \approx 80\%$$

15

(c)

Energy stored in a inductor L carrying

Current i is $U = \frac{1}{2} L i^2$

Rate at which energy is stored

$$= \frac{dU}{dt} = \frac{1}{2} L 2i \left(\frac{di}{dt}\right) = Li \left(\frac{di}{dt}\right)$$

At $t = 0, i = 0, \therefore \frac{dU}{dt} = 0$

At $t = \infty, i = i_0$ (constant), $\therefore \frac{dU}{dt} = 0$

16

(d)

Required time $t = T/4 = \frac{1}{4 \times 50} = 5 \times 10^{-3} \text{ sec}$

17

(a)

Maximum voltage is AC circuit

$$V_0 = 282 \text{ V}$$



$$V = \frac{V_0}{\sqrt{2}} = \frac{282}{\sqrt{2}}$$

$$V = \frac{282}{1.41} = \frac{28200}{141}$$

$$V = 200 \text{ V}$$

18

(b)

$$X_C = \frac{1}{2\pi\nu C} = \frac{1}{0} = \infty$$

19

(b)


$$Z = \sqrt{R^2 + X_L^2} = \sqrt{10^2 + (2\pi \times 60 \times 2)^2} = 753.7$$

$$\therefore i = \frac{120}{753.7} = 0.159 \text{ A}$$

20

(b)

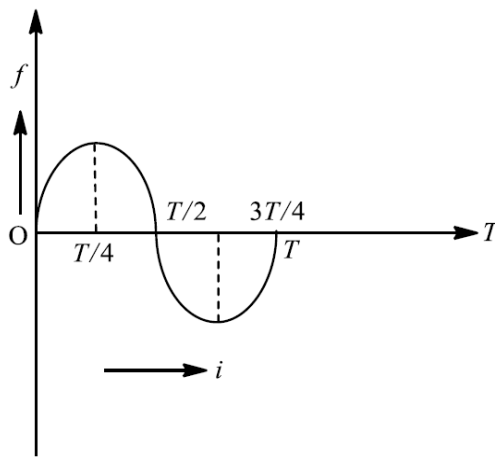An alternating current is one whose magnitude changes continuously with time between zero and a maximum value and whose direction reverses periodically. The relation between frequency (f) and time (T) is.



$$T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s}$$

As is clear from the figure time taken to reach the maximum value is

$$\frac{T}{4} = \frac{0.02}{4} = 0.005 \text{ s}$$

ANSWER-KEY										
Q.	1	2	3	4	5	6	7	8	9	10
A.	B	C	B	A	D	A	B	D	D	B
Q.	11	12	13	14	15	16	17	18	19	20
A.	B	B	A	B	C	D	A	B	B	B



**SMARTLEARN
COACHING**